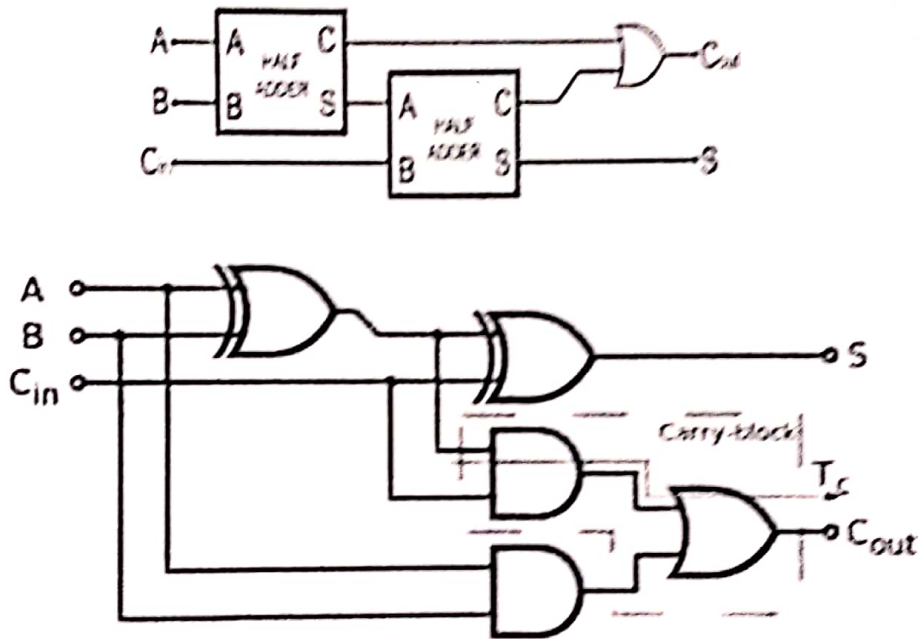


## 2. Full Adder:

The downfall of half adders is that while they can generate a carry out output, they cannot deal with a carry in signal.

A full adder solves this problem by adding three numbers together - the two addends as in the half adder, and a carry in input. The outputs of the full adder are designated as Sum (S) and Carry out (Cout). A block diagram of Full Adder implementation is as follows:



Truth Table:

Inputs			Outputs	
A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

### LAB TASKS

Name Mohammad Yehya Hayati Student ID 21K-3309 Section PCS-26

#### Exercise # 1

Use K-Map to find expression for Carry and Sum for Full Adder. Use Truth Table Given in manual.

	C	Sum			Carry
AB	0	1		AB	0
00	0	1		00	0
01	1	0		01	0
11	0	1		11	1
10	1	0		10	1

$$ABC + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C}$$

$$= C(AB + \bar{A}\bar{B}) + \bar{C}(\bar{A}B + A\bar{B})$$

(XNOR)                  (XOR)

$$= C(\bar{A}B + AB) + \bar{C}(\bar{A}B + AB)$$

C · XOR                  +     $\bar{C}$  · XOR

$$\Rightarrow C \text{ XOR } (A \text{ XOR } B)$$

$$AB + BC + AC$$

#### Exercise # 2

Design and implement Full Adder Circuit on Bread board

#### Exercise # 3

Design and implement Full Subtractor Circuit on Bread board.