




DLD LAB 3(SOFTWARE)

Mohammad Yehya Hayati, 21K-3309, BCS-2G

Table of Contents


Exercise #1:	2
Exercise #2:	3
Exercise #3:	4
Exercise #4:	4
Exercise #5:	5
Exercise #6:	5
Exercise #7:	6
Exercise #8:	6
True/False:	7

Exercise #1:

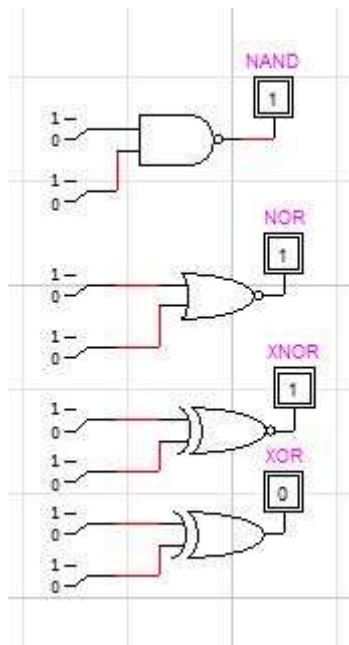


A	B	NAND	NOR	XNOR	XOR
0	0	1	1	1	0
0	1	1	0	0	1
1	0	1	0	0	1
1	1	0	0	1	0

Exercise #2:

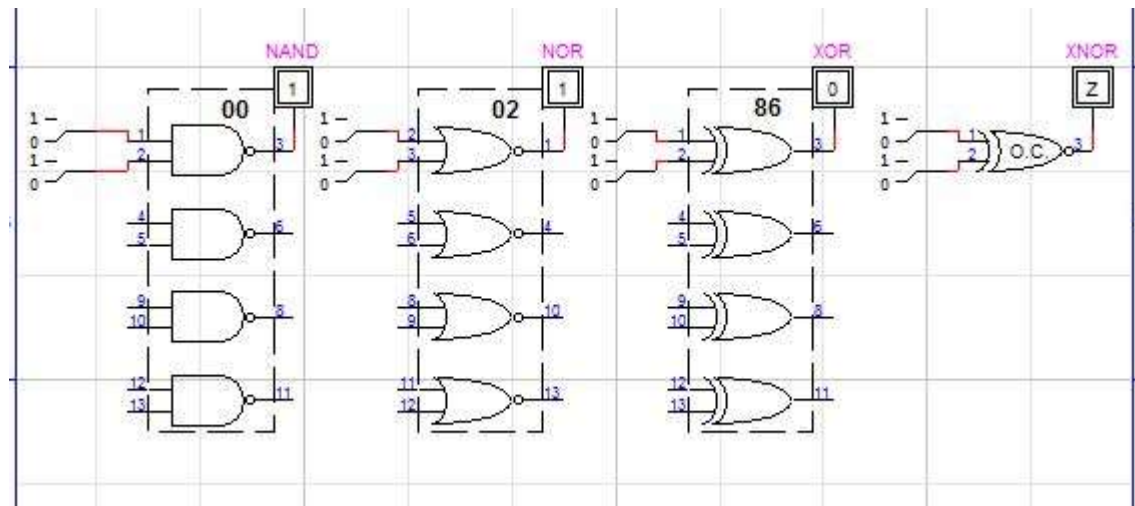


Truth Table is same as the table for Q1

Exercise #3:

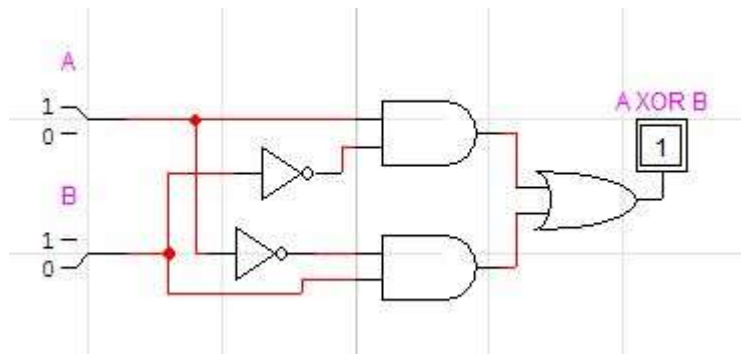


A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

Exercise #4:

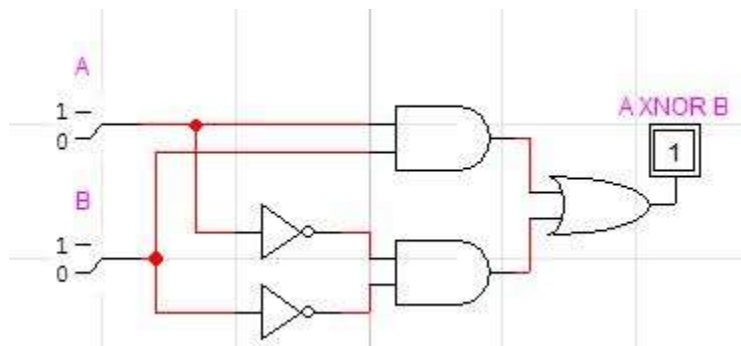


A	B	A XNOR B
0	0	1
0	1	0
1	0	0
1	1	1

Exercise #5:

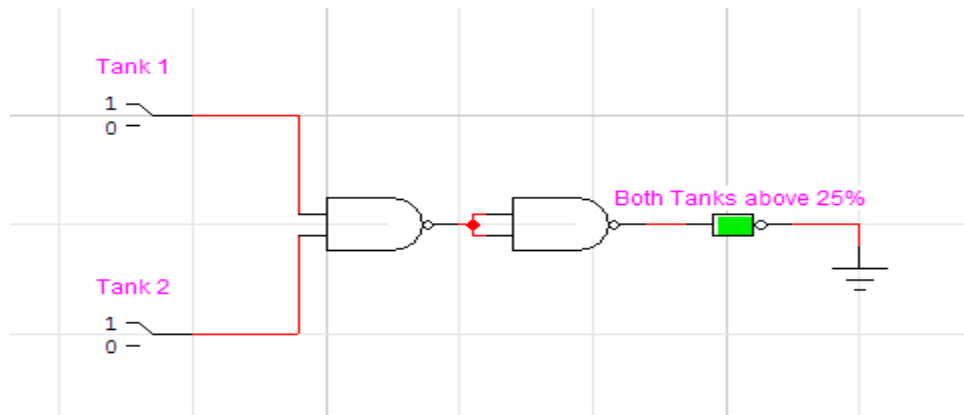


Tank 1	Tank 2	Output (LED-Green)
0	0	Off
0	1	Off
1	0	Off
1	1	On

Exercise #6:

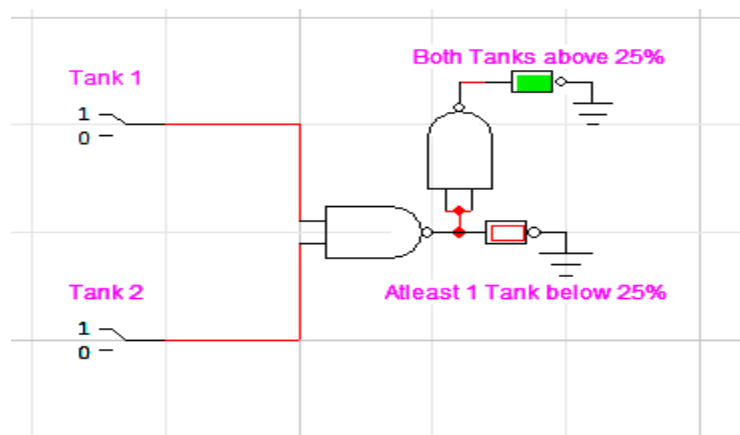


Tank 1	Tank 2	Output (LED-Green)	Output (LED-Red)
0	0	Off	On
0	1	Off	On
1	0	Off	On
1	1	On	Off

Exercise #7:

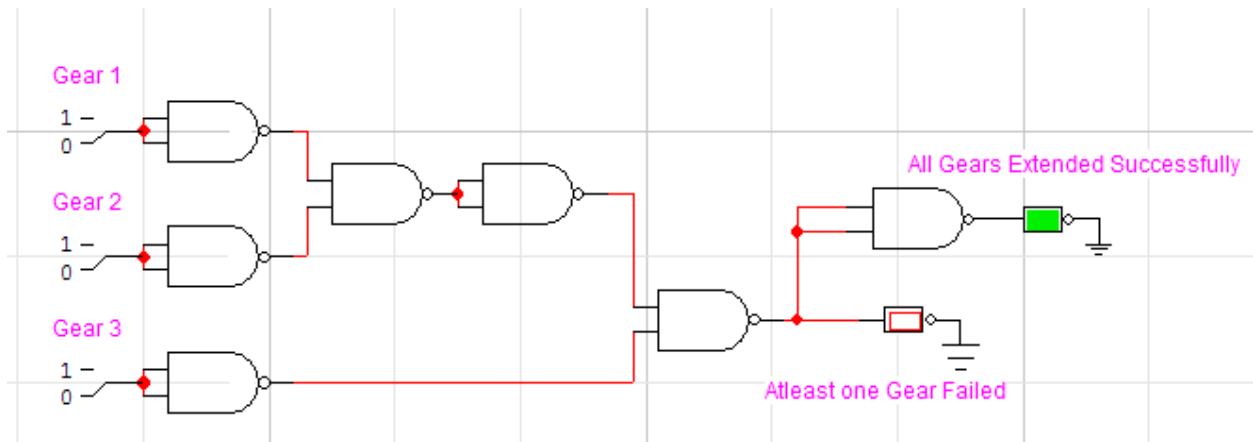


Gear 1	Gear 2	Gear 3	Output (LED-Green)	Output (LED-Red)
0	0	0	On	Off
0	0	1	Off	On
0	1	0	Off	On
0	1	1	Off	On
1	0	0	Off	On
1	0	1	Off	On
1	1	0	Off	On
1	1	1	Off	On

Exercise #8:

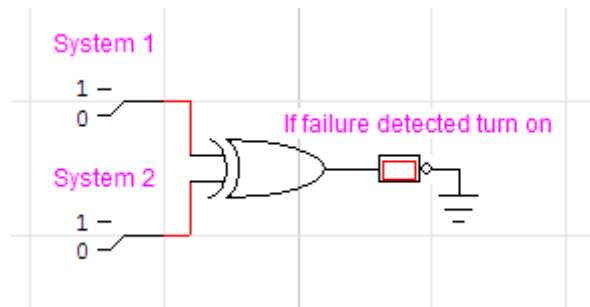

Same as above but using NAND, NOR

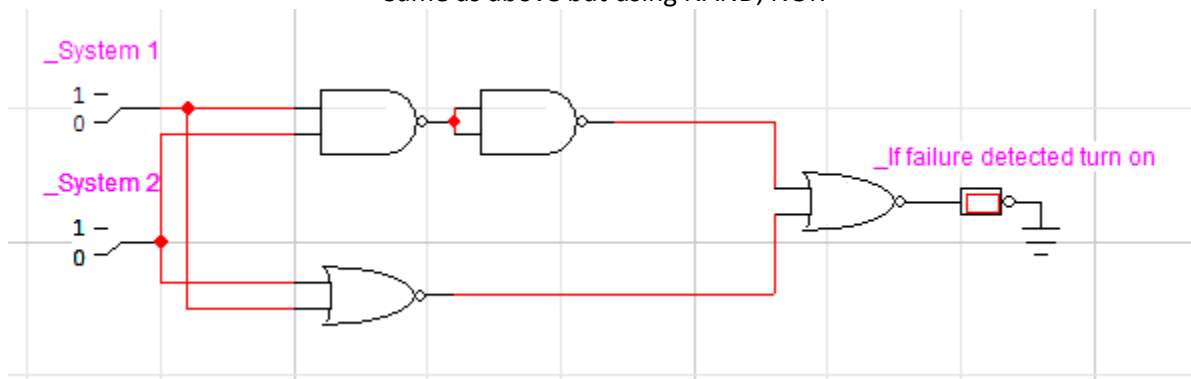

System 1	System 2	Output (LED-Red)
0	0	0
0	1	1
1	0	1
1	1	0

True/False:

1.True

2.True

3.False

4.False

5.True

6.True

7.False