

Put the laundry away,
baby. You don't need
no clean socks ... it's
Flipflop season.

LATCHES, FLIPS FLOPS & TIMERS


CHAPTER 7



Sumaiyah Zahid

LATCHES


Memory storage device

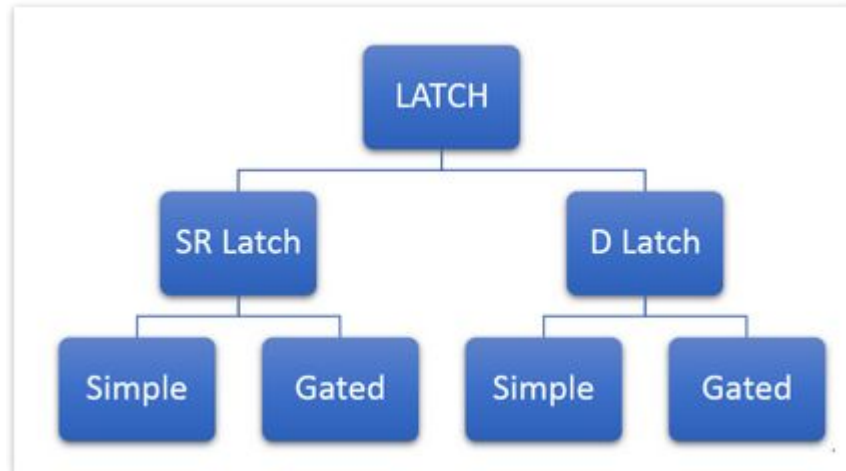


S-R (SET-RESET) LATCH

SET means that the Q output is HIGH.

RESET means that the Q output is LOW.

 


(a) Active-HIGH input S-R latch

 

(b) Active-LOW input \bar{S} - \bar{R} latch

S-R (SET-RESET) LATCH

 

(a) Active-HIGH input S-R latch

S-R (SET-RESET) LATCH

Case 1: $S=1, R=0, Q=1, Q'=0$

$S=0, R=0, Q=1, Q'=0$ (Memory)


Case 2: $S=0, R=1, Q=0, Q'=1$

$S=0, R=0, Q=0, Q'=1$ (Memory)

Case 3: $S=1, R=1, Q=0, Q'=0$ (Invalid)

$S=0, R=0, Q=0, Q'=1$


$S=0, R=0, Q=1, Q'=0$

 





(a) Active-HIGH input S-R latch

S-R (SET-RESET) LATCH

| S | R | Q | Q' |
|---|---|-----------|-----------|
| 0 | 0 | No Change | No Change |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | Invalid | Invalid |

 


(a) Active-HIGH input S-R latch

    

S-R (SET-RESET) LATCH

| S | R | Q | Q' |
|---|---|-----------|-----------|
| 0 | 0 | Invalid | Invalid |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | No Change | No Change |

 


(b) Active-LOW input \bar{S} - \bar{R} latch

S-R (SET-RESET) LATCH

Home Task:

Verify all the cases for Active Low SR Latch.
 
<https://www.youtube.com/watch?v=kt8dCYWGH4>




(b) Active-LOW input \bar{S} - \bar{R} latch


S-R (SET-RESET) LATCH

 EXAMPLE 7-1

If the \bar{S} and \bar{R} waveforms in Figure 7-5(a) are applied to the inputs of the latch in Figure 7-4(b), determine the waveform that will be observed on the Q output. Assume that Q is initially LOW.




GATED SR LATCH (ACTIVE HIGH)

 


| E | S | R | Q | \bar{Q} |
|---|---|---|-------|-----------|
| 0 | 0 | 0 | latch | latch |
| 0 | 0 | 1 | latch | latch |
| 0 | 1 | 0 | latch | latch |
| 0 | 1 | 1 | latch | latch |
| 1 | 0 | 0 | latch | latch |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |

GATED SR LATCH (ACTIVE HIGH)

 

(a) Logic diagram

 

(b) Logic symbol

FIGURE 7-8 A gated S-R latch.

GATED SR LATCH (ACTIVE HIGH)

EXAMPLE 7-2

Determine the Q output waveform if the inputs shown in Figure 7-9(a) are applied to a gated S-R latch that is initially RESET.



 


FIGURE 7-9

GATED D LATCH

 

(a) Logic diagram

 

(b) Logic symbol

$D = \text{HIGH} \ \& \ EN = \text{HIGH}$, the latch will set.


$D = \text{LOW} \ \& \ EN = \text{HIGH}$, the latch will reset.

Stated another way, the output Q follows the input D when EN is HIGH.

GATED D LATCH

 
EXAMPLE 7-3

Determine the Q output waveform if the inputs shown in Figure 7-11(a) are applied to a gated D latch, which is initially RESET.




CLOCK

A periodic signal.

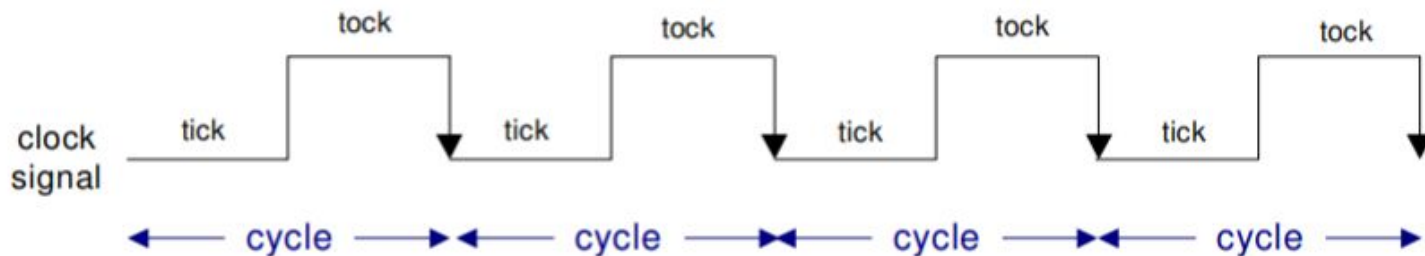

- In our jargon, a clock cycle = *tick*-phase (low), followed by a *tock*-phase (high)

CLOCK

 

$$\text{Period} = 1 / \text{Frequency}$$

$$\text{Period} = T_{on} + T_{off}$$

$$\text{Duty Cycle} = T_{on} / (T_{on} + T_{off}) * 100$$

(On Percentage)

50% duty cycle




75% duty cycle




25% duty cycle



CLOCK

 


CLOCK

 

FLIPS FLOPS



Flip-flops are edge-triggered or edge-sensitive devices.

 Output changes state only at a specified point (leading or trailing edge) on the triggering input called the clock (CLK).




SR FLIP FLOP


| CLK | S | R | Q | Q' |
|-----|---|---|---------|---------|
| ↓ | X | X | Q(n-1) | Q'(n-1) |
| ↑ | 0 | 0 | Q'(n-1) | Q'(n-1) |
| ↑ | 0 | 1 | 0 | 1 |
| ↑ | 1 | 0 | 1 | 0 |
| ↑ | 1 | 1 | Invalid | Invalid |

  

D FLIP FLOP

 

 
(a) $D = 1$ flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



(b) $D = 0$ flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)

D FLIP FLOP


| CLK | D | Q | Q' |
|-----|---|----------|-----------|
| ↓ | X | $Q(n-1)$ | $Q'(n-1)$ |
| ↑ | 1 | 1 | 0 |
| ↑ | 0 | 0 | 1 |

 

D FLIP FLOP

 EXAMPLE 7-4

Determine the Q and \bar{Q} output waveforms of the flip-flop in Figure 7-15 for the D and CLK inputs in Figure 7-16(a). Assume that the positive edge-triggered flip-flop is initially RESET.




LIMITATIONS OF D AND SR FLIP FLOP

D has only single input.

SR flip flop has an invalid state.



JK FLIP FLOP

 

JK FLIP FLOP

Case 1: CLK=0 (Memory)

Case 2: CLK=1, J=1, K=0, Q=1, Q'=0

Case 3: CLK=1, J=0, K=1, Q=0, Q'=1


Case 4: CLK=1, J=1, K=1,

$Q(n)=0, Q'(n)=1, Q(n+1)=1, Q'(n+1)=0$


$Q(n)=1, Q'(n)=0, Q(n+1)=0, Q'(n+1)=1$

JK FLIP FLOP


| CLK | J | K | Q | Q' |
|-----|---|---|-----------|-----------|
| ↓ | X | X | $Q(n-1)$ | $Q'(n-1)$ |
| ↑ | 0 | 0 | $Q'(n-1)$ | $Q'(n-1)$ |
| ↑ | 0 | 1 | 0 | 1 |
| ↑ | 1 | 0 | 1 | 0 |
| ↑ | 1 | 1 | Toggles | Toggles |

 


JK FLIP FLOPS

 

 
(a) $J = 1, K = 0$ flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



 (b) $J = 0, K = 1$ flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)



 (c) $J = 1, K = 1$ flip-flop changes state (toggle).



(d) $J = 0, K = 0$ flip-flop does not change. (If SET, it remains SET; if RESET, it remains RESET.)

JK FLIP FLOPS

TABLE 7-3

Truth table for a positive edge-triggered J-K flip-flop.

| Inputs | | | Outputs | | Comments |
|--------|-----|-----|-------------|-------------|-----------|
| J | K | CLK | Q | \bar{Q} | |
| 0 | 0 | ↑ | Q_0 | \bar{Q}_0 | No change |
| 0 | 1 | ↑ | 0 | 1 | RESET |
| 1 | 0 | ↑ | 1 | 0 | SET |
| 1 | 1 | ↑ | \bar{Q}_0 | Q_0 | Toggle |



↑ = clock transition LOW to HIGH

Q_0 = output level prior to clock transition


JK FLIP FLOP

 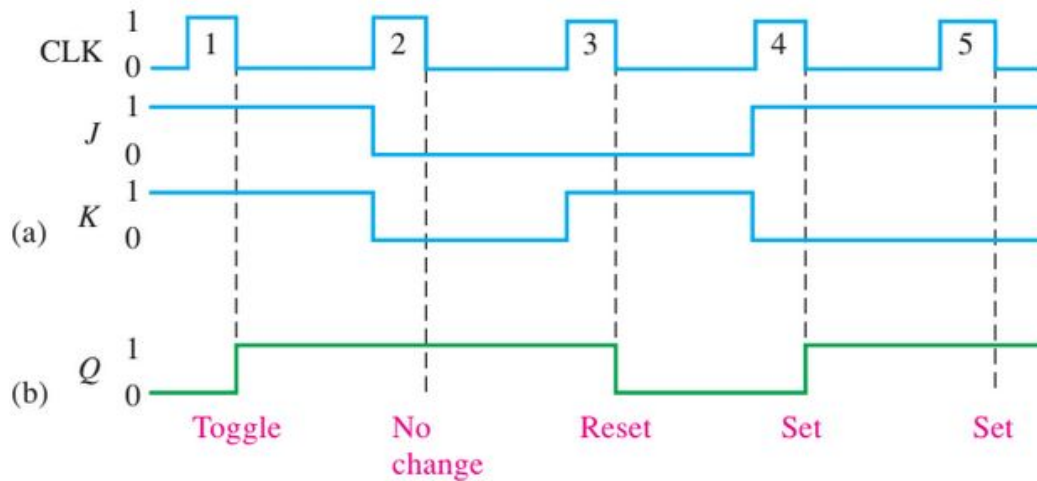EXAMPLE 7-5

The waveforms in Figure 7–18(a) are applied to the J , K , and clock inputs as indicated. Determine the Q output, assuming that the flip-flop is initially RESET.





MASTER SLAVE JK FLIP FLOP

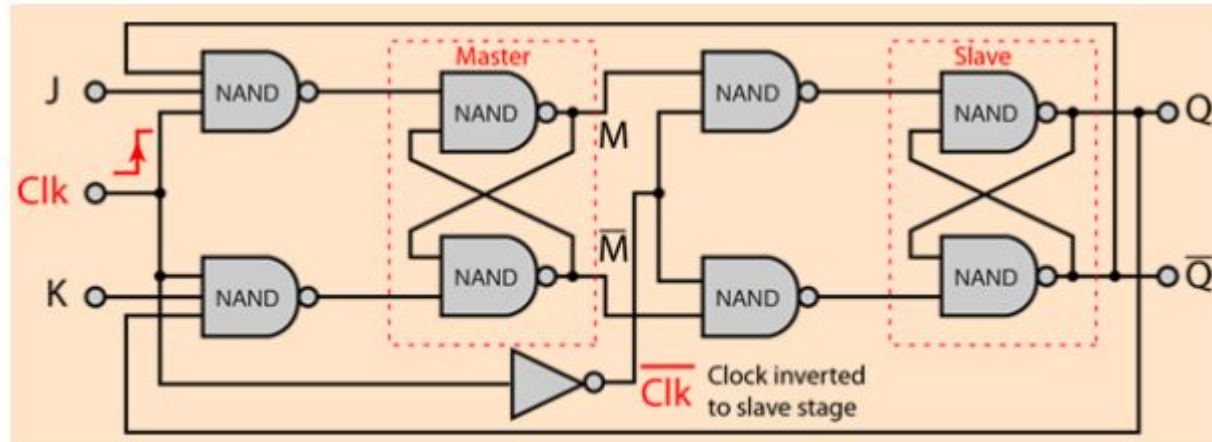



Master Slave JK Flip Flop

MASTER SLAVE JK FLIP FLOP

J-K flip-flop races when clock high.

  


  Master-slave arrangement suppresses racing.




EDGE TRIGGERING

D Flip Flop

 

 (a) A simplified logic diagram for a positive edge-triggered D flip-flop



(b) A type of pulse transition detector

FIGURE 7-19 Edge triggering.

EDGE TRIGGERED - D FLIP FLOP

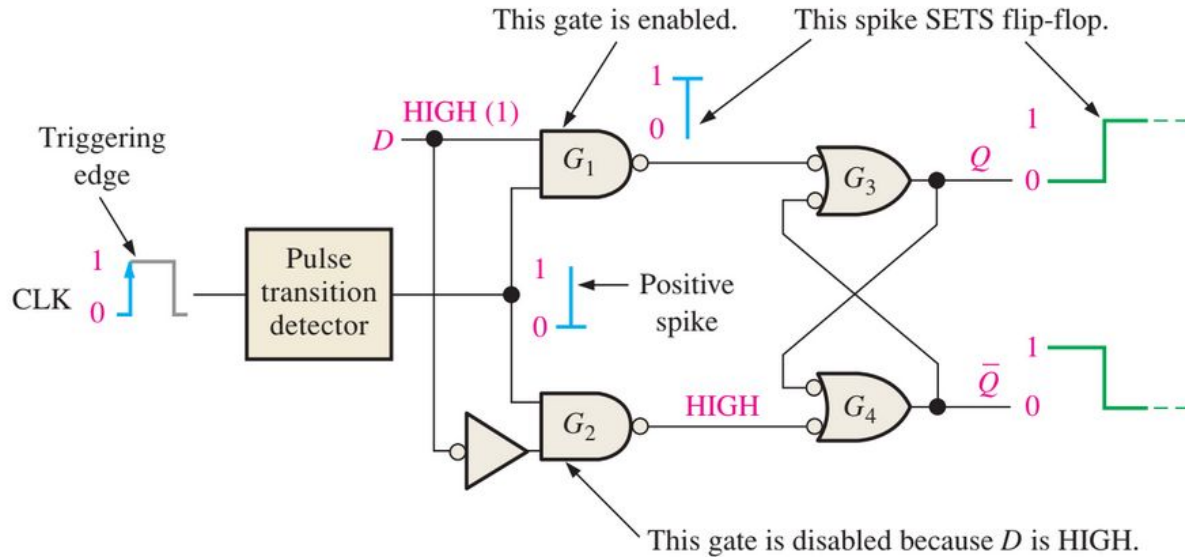


FIGURE 7-20 Flip-flop making a transition from the RESET state to the SET state on the positive-going edge of the clock pulse.

EDGE TRIGGERED - D FLIP FLOP

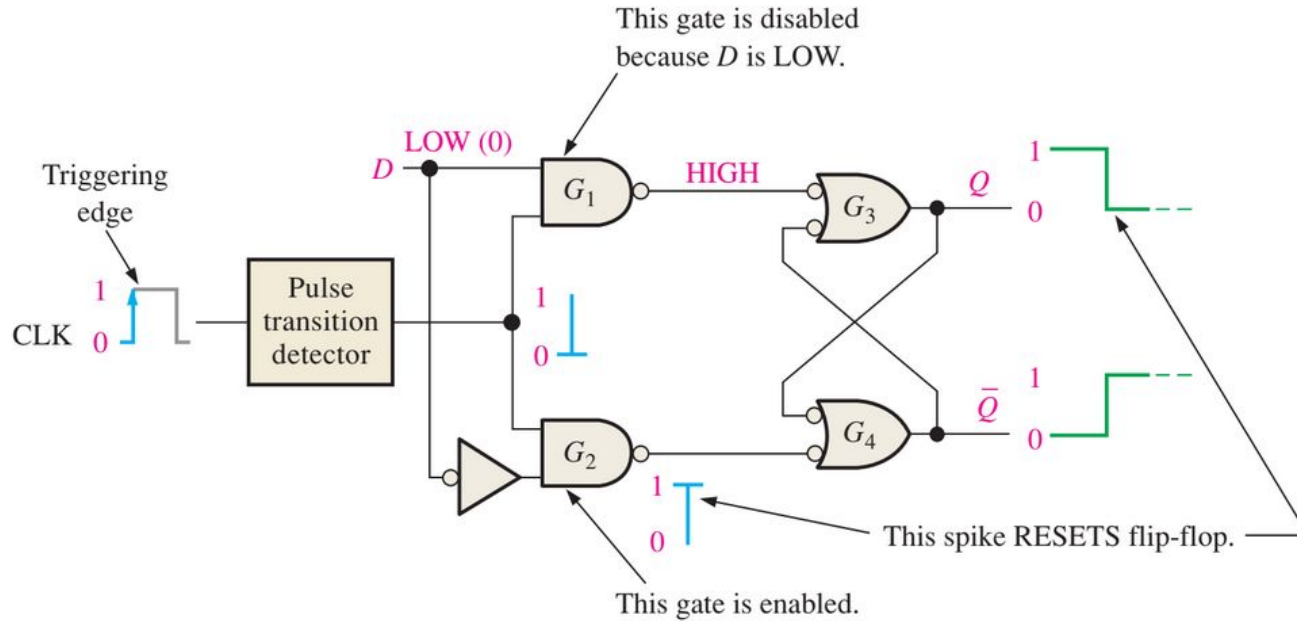


FIGURE 7-21 Flip-flop making a transition from the SET state to the RESET state on the positive-going edge of the clock pulse.

EDGE TRIGGERED - JK FLIP FLOP

 


FIGURE 7-23 A simplified logic diagram for a positive edge-triggered J-K flip-flop.

EDGE TRIGGERED - JK FLIP FLOP

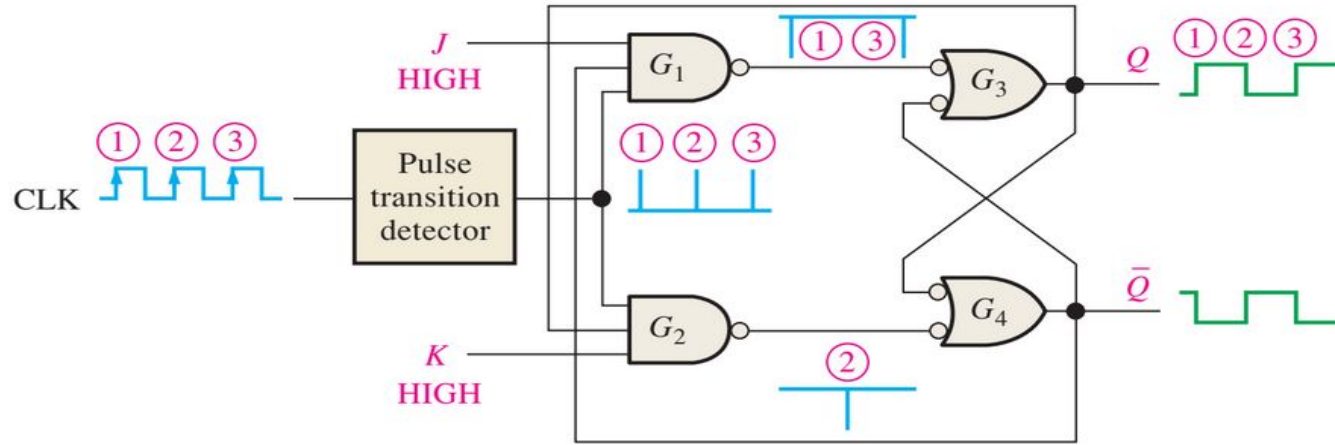


FIGURE 7-24 Transitions illustrating flip-flop operation.

A J-K flip-flop connected for toggle operation is sometimes called a T flip-flop.

SYNCHRONOUS VS ASYNCHRONOUS INPUTS

D and J-K inputs are called synchronous inputs, because the data transferring is synchronised with the clock.

Asynchronous inputs affect the state of the flip-flop independent of the clock.

Preset (PRE) and Clear (CLR)

OR

Direct set (SD) and Direct reset (RD)

SYNCHRONOUS VS ASYNCHRONOUS INPUTS

 


FIGURE 7-25 Logic symbol for a D flip-flop with active-LOW preset and clear inputs.


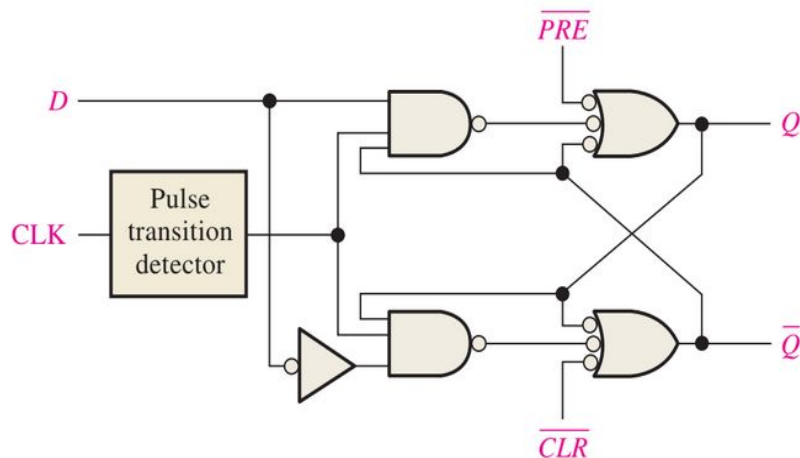
 


FIGURE 7-26 Logic diagram for a basic D flip-flop with active-LOW preset and clear inputs.

SYNCHRONOUS VS ASYNCHRONOUS INPUTS

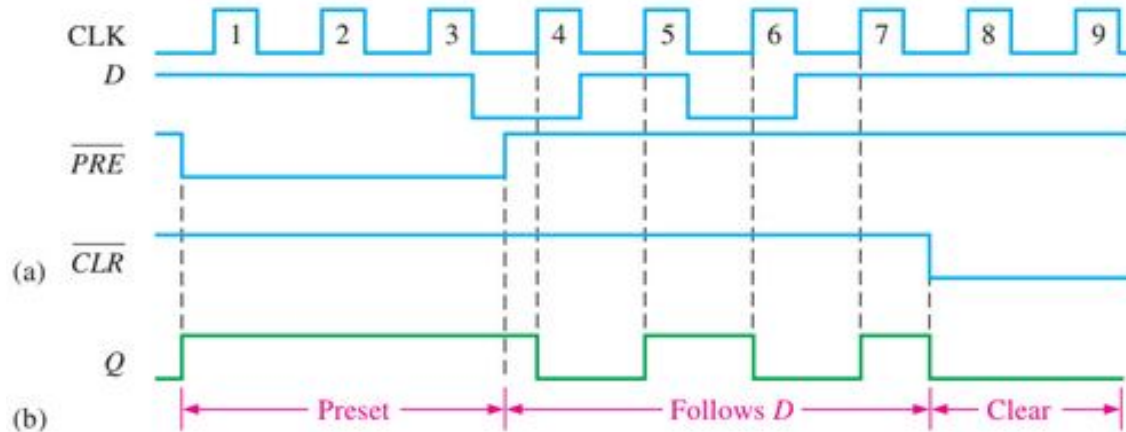For the positive edge-triggered D flip-flop with preset and clear inputs in Figure, determine the Q output for the inputs shown in the timing diagram in part (a) if Q is initially LOW.



FLIP FLOP APPLICATIONS

Parallel Data Storage

This group of four flip-flops is an example of a basic register used for data storage.

 
 


FIGURE 7-35 Example of flip-flops used in a basic register for parallel data storage.

FLIP FLOP APPLICATIONS

Frequency Division

A single flip-flop can be applied as a divide-by-2 device.


 
 


FIGURE 7-36 The D flip-flop and J-K flip-flop as a divide-by-2 device. Q is one-half the frequency of CLK. Open file F07-36 and verify the operation.

FLIP FLOP APPLICATIONS

Frequency Division

 Further division of a clock frequency can be achieved by using the output of one flip-flop as the clock input to a second flip-flop.




FLIP FLOP APPLICATIONS

Counters

J-K flip-flops used to generate a binary count sequence (00,01,10,11).

Two repetitions are shown.

 

HOME TASK

Design a counter which can count from 0 through 15.

Reading Task : 7-3 Flip-Flop Operating Characteristics