

# Digital Logic Design

## (EL-1005)

### LABORATORY MANUAL

### Spring 2022



## LAB 08

### Binary Comparator

Instructor: Engr. Misbah Malik

---

STUDENT NAME

---

ROLL NO

---

SEC

---

FACULTY'S SIGNATURE & DATE

**MARKS AWARDED: /02**

---

NATIONAL UNIVERSITY OF COMPUTER AND EMERGING SCIENCES (FAST-NUCES), KARACHI

---

## Lab Session 08: Binary Comparator

---

**OBJECTIVES:**

- To learn and understand how to design a multiple output combinational circuit
- To learn and understand the working of 2-bit binary comparator
- To learn and understand the working and usage of Exclusive-OR and Exclusive-NOR gates

**APPARATUS:** Logic trainer, Logic probe

**COMPONENTS:** ICs 74LS08, 74LS32, 74LS04, 74LS86, 74LS02

**THEORY:**

Binary comparator is a combinational circuit that compares magnitude of two binary data signals A & B and generates the results of comparison in the form of three output signals  $A > B$ ,  $A = B$ ,  $A < B$ . Binary comparator is a multiple input and multiple output combinational circuit. When a combinational circuit has two or more than two outputs then each output is expressed separately as a function of all inputs. Separate K-map is made for each output.

**One-bit comparator:**

One-bit comparator compares magnitude of two numbers A and B, 1 bit each, and generates the comparison result. The result consists of three outputs let us say L, E, G, so that

$$L = 1 \text{ if } A < B$$

$$E = 1 \text{ if } A = B$$

**Truth Table:**

$$G = 1 \text{ if } A > B$$

Inputs		Outputs		
A	B	L	E	G
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

### K-Maps for Outputs:

		B	
		0	1
A	0		1
	1		

K-Map for Output L

		B	
		0	1
A	0	1	
	1		1

K-Map for Output E

		B	
		0	1
A	0		
	1	1	

K-Map for Output G

### Boolean Expressions of Outputs:


L:  $\bar{A}B$

E:  $AB + \bar{A}\bar{B}$


G:  $A\bar{B}$
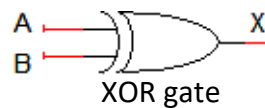
### Exclusive-OR & Exclusive-NOR gates:


The figure given below shows the symbol of Exclusive-OR (XOR) and Exclusive-NOR (XNOR) gates.



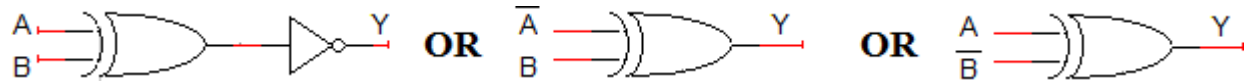Boolean expression of XNOR gate is  $AB + \bar{A}\bar{B}$  and Boolean expression of XOR is  $\bar{A}B + A\bar{B}$ . Boolean expression of XNOR gate can be implemented using XOR gate as shown in figure below:



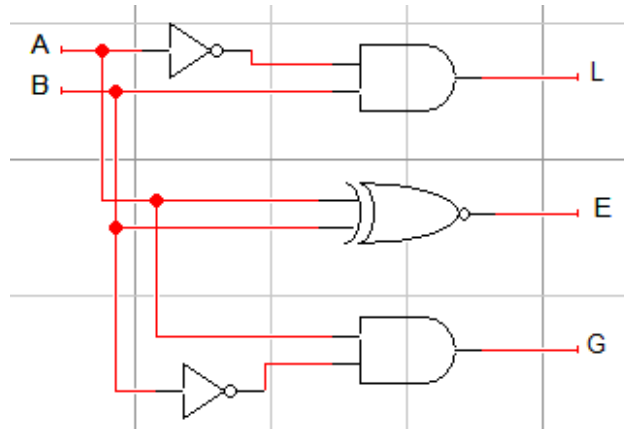**Circuit Diagram for one-bit comparator:**




In this experiment 74LS86 IC will be used for implementation of XOR gate function. 74LS86 IC contains four 2-input XOR gates. The function table and connection diagram for this IC are shown below:

**Function Table:**

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	L

H= Logic High, L= Logic Low

**Connection Diagram:**

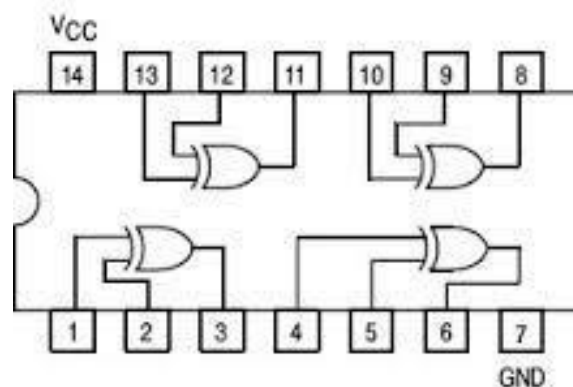

## LAB TASKS

Name \_\_\_\_\_ Student ID \_\_\_\_\_ Section \_\_\_\_\_

### Exercise # 1

Design a combinational circuit that compares two 2-bit numbers and generates the comparison result. The result consists of three outputs let us say L, E, G, so that

$$L = 1 \text{ if } A < B$$

$$E = 1 \text{ if } A = B$$

$$G = 1 \text{ if } A > B$$

#### 1. Write truth table

**Exercise # 2**

Find minimal SOP expressions for the outputs L, E, and G using K-map. Draw separate K-map for each output in the space given below

**Exercise # 3**

Implement the combinational circuit of 2-Bit Binary comparator on Logisim and generate truth table.

**INSTRUCTION FOR SUBMISSION**

**Upload Word File with all working on Google Classroom.**