
HI...

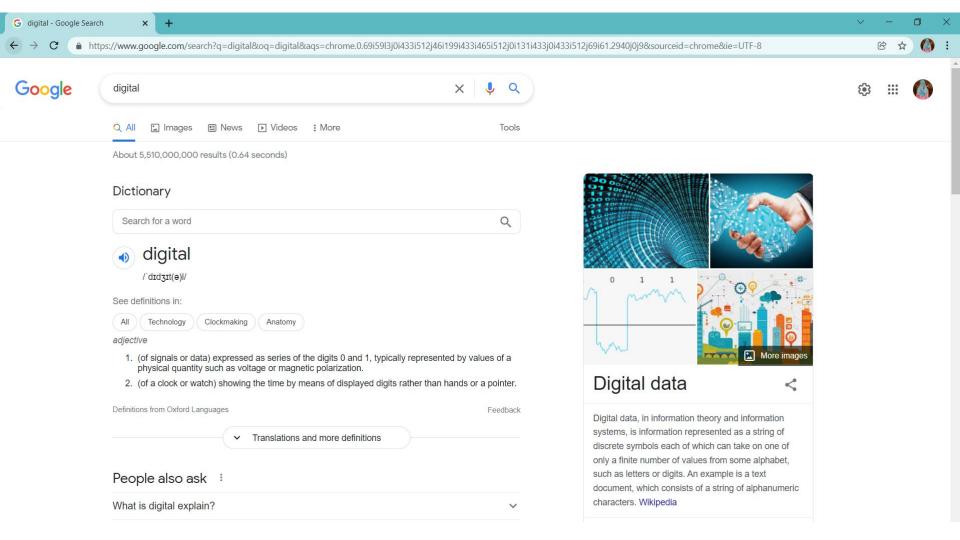


I AM SUMAIYAH

DIGITAL LOGIC DESIGN

It's as easy as 01, 10, 11




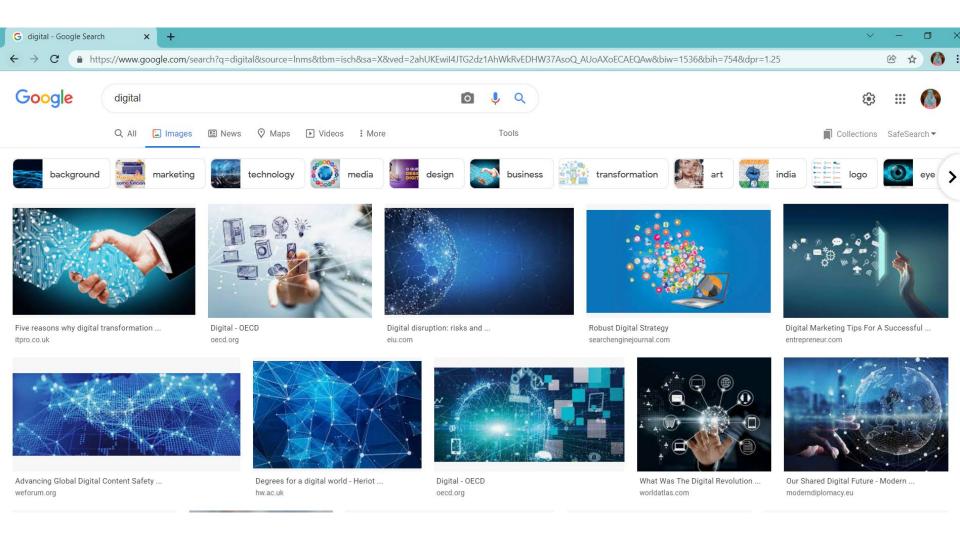


ANALOG VS DIGITAL

An analog quantity has continuous values.

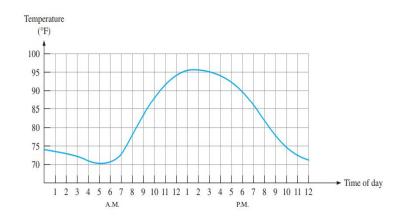A digital quantity has discrete set of values.



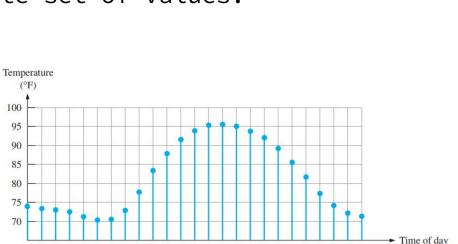

P.M.

9 10 11 12 1 2 3 4

A.M.




DIGITAL ADVANTAGE

It can be processed and transmitted more efficiently.

It can be stored more compactly and reproduced with greater accuracy.

Less prone to noise.

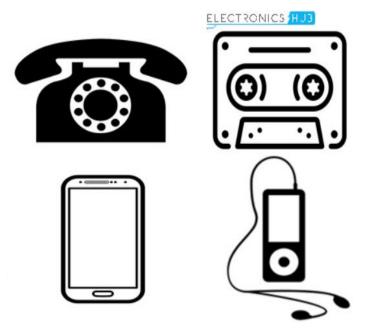

Each Smart Watch is a Digital Watch.

Each Smart Phone is a Digital Phone.

Each Smart City is a Digital City.

SMART is just advanced DIGITAL.

BINARY DIGITS

There are two digits in the binary system, 1 and 0. Each digit is called a bit.

Binary + Digit = Bit

There are only 10

types of people

in the world:

Those who understand binary
and those who don't.

BINARY DIGITS

Positive Logic:

```
High = 1
```

Low =
$$0$$

Negative Logic:

```
High = 0
```


Low =
$$1$$

LOGIC LEVELS


The voltages used to represent a 1 and a 0 are called logic levels.'

LOW = < 0.8 V

HIGH = 2V - 3.3 V

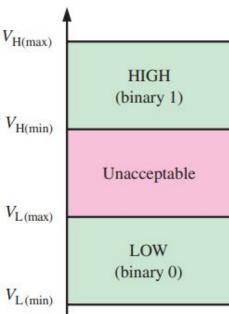

LOGIC GATES - NOT GATE

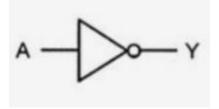


INPUT	OUTDUT	
Α	OUTPUT	
0	1	
1	0	





LOGIC GATES - AND GATE



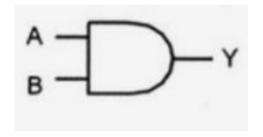

Α	В	
0	0	0
1	0	0
0	1	0
1	1	1

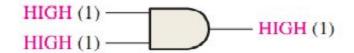


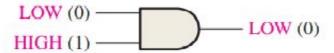





LOGIC GATES - OR GATE



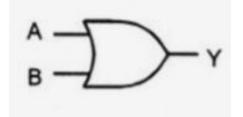


INPUT		OUTDUT
Α	В	OUTPUT
0	0	0
1	0	1
0	1	1
1	1	1

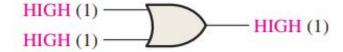

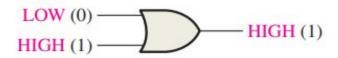

DIGITAL WAVEFORMS

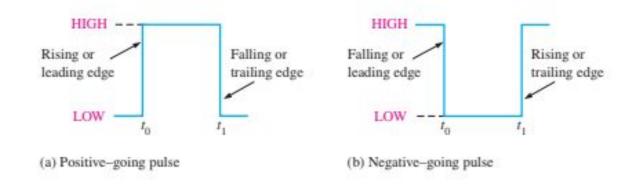
It consist of voltage levels that are changing back and forth between the HIGH and LOW levels or states.



PERIODIC AND NON-PERIODIC WAVES

A periodic pulse waveform is one that repeats itself at a fixed interval, called a period (T).

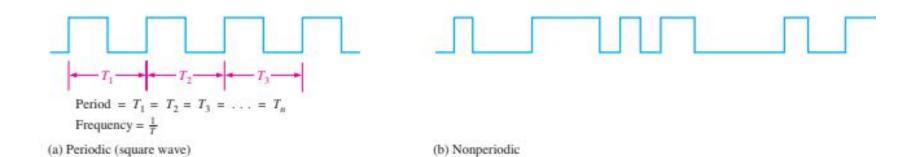The frequency (f) is the rate at which it repeats itself and is measured in hertz (Hz).



WAVEFORM CHARACTERISTICS

The frequency (f) of a pulse $f = \frac{1}{T}$ (digital) waveform is the reciprocal of the period. $T = \frac{1}{T}$

Equation 1-1

Equation 1-2

Duty Cycle: It is the ratio of the pulse width (tW) to the period (T).

Duty cycle =
$$\left(\frac{t_W}{T}\right)$$
100%

Equation 1-3

CLOCK

The clock is a periodic waveform in which each interval between pulses (the period) equals the time for one bit.



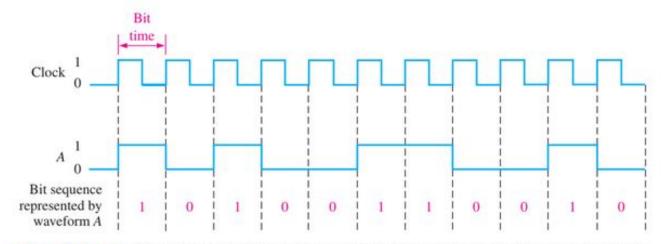


FIGURE 1–11 Example of a clock waveform synchronized with a waveform representation of a sequence of bits.


TIMING DIAGRAMS

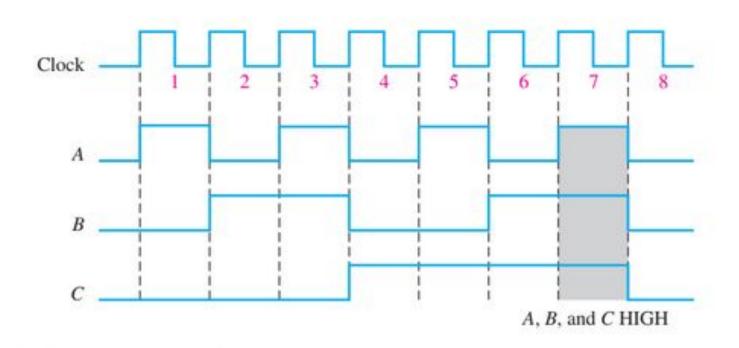

DATA TRANSFER

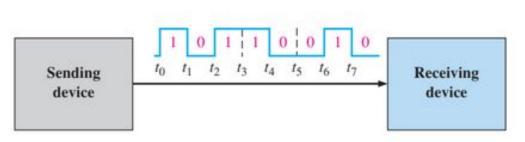

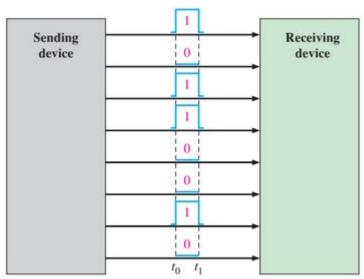(a) Serial transfer of 8 bits of binary data. Interval t_0 to t_1 is first.



(b) Parallel transfer of 8 bits of binary data. The beginning time is t_0 .

- (a) Determine the total time required to serially transfer the eight bits contained in waveform A of Figure 1–14, and indicate the sequence of bits. The left-most bit is the first to be transferred. The 1 MHz clock is used as reference.
- (b) What is the total time to transfer the same eight bits in parallel?

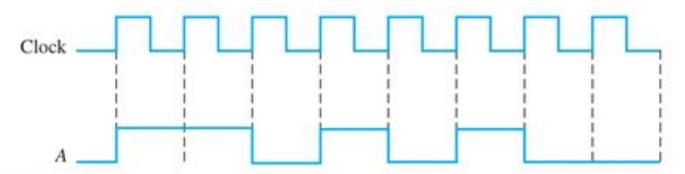


FIGURE 1-14

Since the frequency of the clock is 1 MHz, the period is

$$T = \frac{1}{f} = \frac{1}{1 \text{ MHz}} = 1 \,\mu\text{s}$$

It takes 1 μ s to transfer each bit in the waveform. The total transfer time for 8 bits is

$$8 \times 1 \,\mu s = 8 \,\mu s$$



FIGURE 1-15

(b) A parallel transfer would take $1 \mu s$ for all eight bits.